
 


## EE201 Flip-Flop Worksheet

 
1. Complete the characteristic table and timing diagram for the following level triggered RS Latch. Q is initially at logic 0. Under “Action,” for each row insert one of the following: a) don’t change, b) toggle, c) set , d) reset, e) undefined




<i>RS Flip-Flop</i>			
S	R	$Q_{t+1}$	Action
0	0	$Q_t$	a) don't change
0	1		
1	0		
1	1		



 
2. Complete the characteristic table and timing diagram for the following edge triggered JK Flip-Flop. Under “Action,” for each row insert one of the following: a) don’t change, b) toggle, c) set , d) reset, e) undefined. Both preset and clear signals are asynchronous with respect to the clock.




<i>JK Flip-Flop</i>			
J	K	$Q_{t+1}$	Action
0	0		
0	1		
1	0		
1	1		

 

 
3. Complete the characteristic table and timing diagram for the following edge triggered T Flip-Flop. Q is initially at logic 0. Under "Action," for each row insert one of the following: a) don't change, b) toggle, c) set, d) reset, e) undefined



<i>T Flip-Flop</i>		
T	$Q_{t+1}$	Action
0		
1		

 

 4. Complete the characteristic table and timing diagram for the following edge triggered D Flip-Flop. Q is initially at logic 0. Under "Action," for each row insert one of the following: a) don't change, b) toggle, c) set, d) reset, e) undefined



<i>D Flip-Flop</i>		
D	$Q_{t+1}$	Action
0		
1		

